

Electric Fields, Circuits

Electric Fields;
*Emf, Currents, Potential
Difference and Multiloop
Circuits*

Lecture 21

الرياضيات والفيزياء العراقي

خاص بمنتهى

Coulomb's Law

$$|F| = \frac{1}{4\pi\epsilon_0} \frac{|q_1||q_2|}{r^2}$$

$$\frac{1}{4\pi\epsilon_0} = 8.99 \times 10^9 \text{ N}\cdot\text{m}^2/\text{C}^2$$

Direction is determined by opposites attract and like charges repel one another.

Recall the Coulomb Force Problem on Two Charges



What is the force on q_o due to q if $q = 2 \text{ C}$, $q_o = 3 \text{ C}$ and the distance between them is 3 meters?

How about if $q_o = 3 \text{ C}$?

How about if $q_o = 1.5 \text{ C}$? $\left| F_{\text{on } q_o \text{ due to } q} \right| = \frac{1}{4\pi\epsilon_0} \frac{|q||q_o|}{r^2}$

Calculating the force exerted by q on any given charge you might place at the location of q_o gets repetitive. The only thing that changes is the value of q_o .

The Electric Field

$$\vec{\mathbf{E}}_q = \frac{\vec{\mathbf{F}}_{qq_o}}{q_o}$$


- We define the electric field associated with a charge or charge distribution to be the electrostatic force exerted per unit of charge on which the force acts.
- If we know \mathbf{E} , the force, \mathbf{F} , on any charge, q_o , is then given by:
- We can calculate \mathbf{E} once and then get \mathbf{F} for any charge easily.

$$\vec{\mathbf{F}}_{qq_o} = q_o \vec{\mathbf{E}}_q$$

The Electric Field

$$\vec{\mathbf{E}} = \frac{\vec{\mathbf{F}}}{q_0}$$

- From a point charge q , the force on q_0 is,
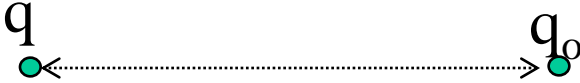
$$|F| = \frac{1}{4\pi\epsilon_0} \frac{|q||q_0|}{r^2}$$


- Then, at q_0 's location, the field associated with q is

$$|E| = \frac{|F|}{|q_0|} = \frac{1}{4\pi\epsilon_0} \frac{|q|}{r^2}$$

- Field is a vector. The direction is away from a positive q and toward a negative q . It is also always in the direction of \mathbf{F} on a positive charge.

$$\vec{\mathbf{F}} = q_0 \vec{\mathbf{E}}$$

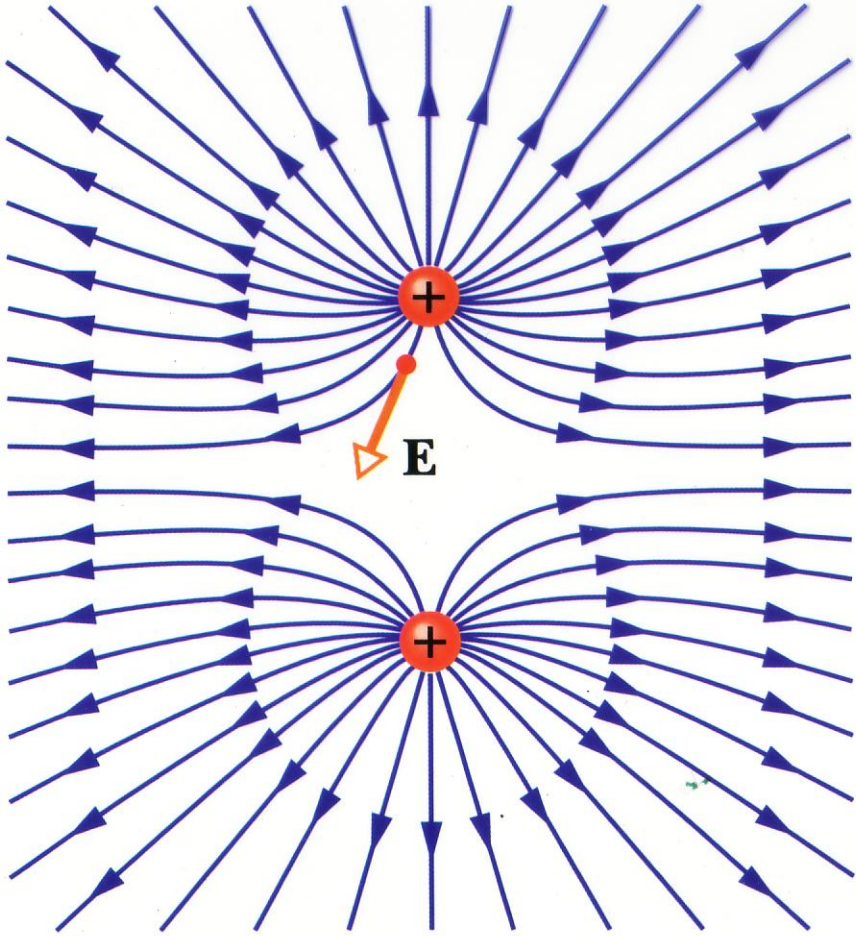


Figure 23-4


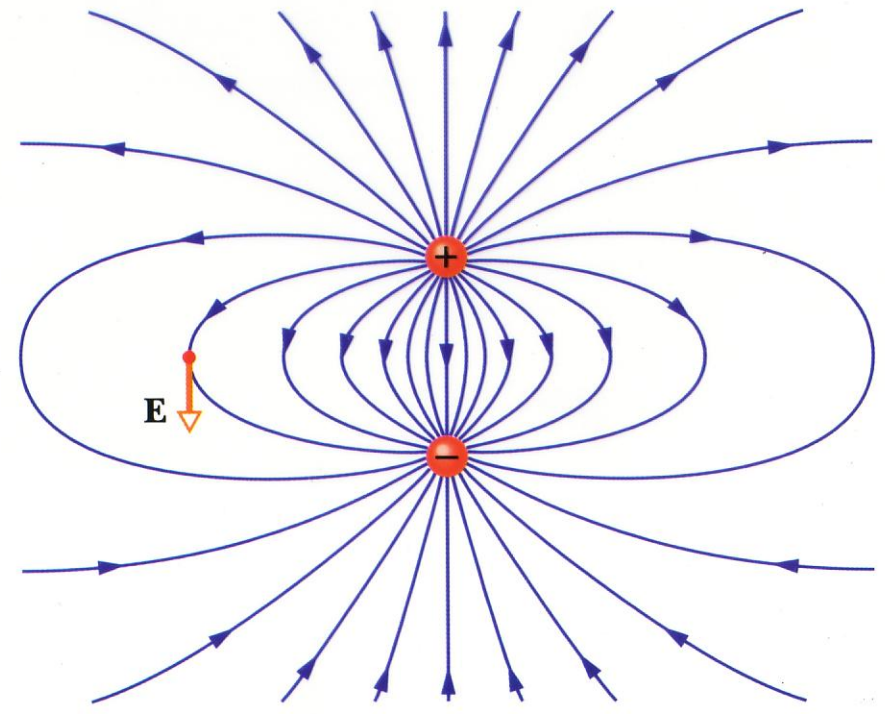
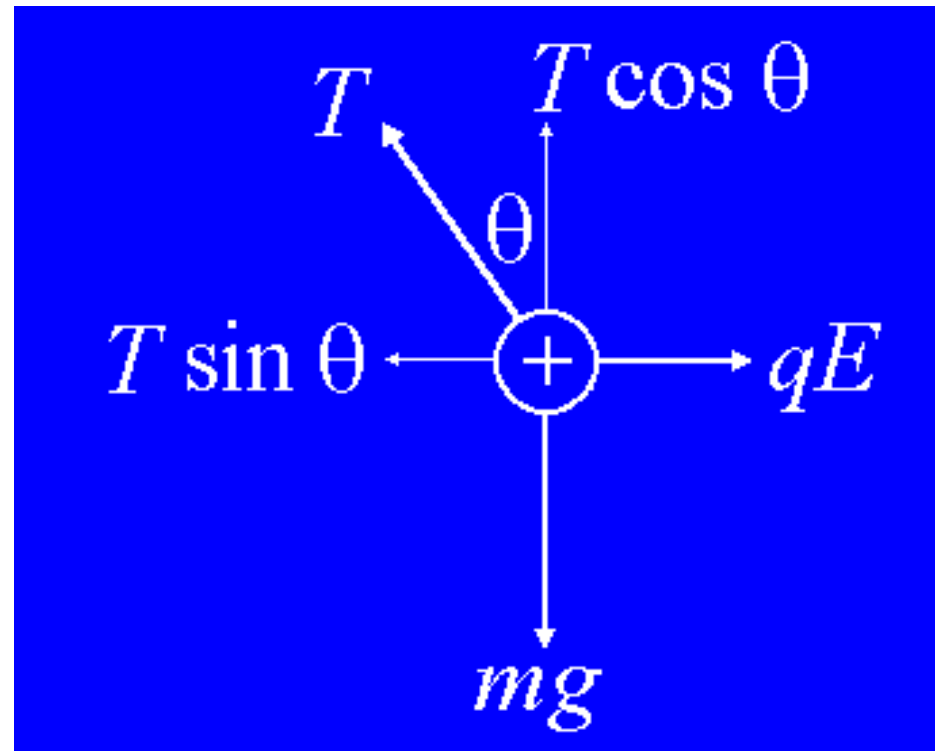


Figure 23-5

Example

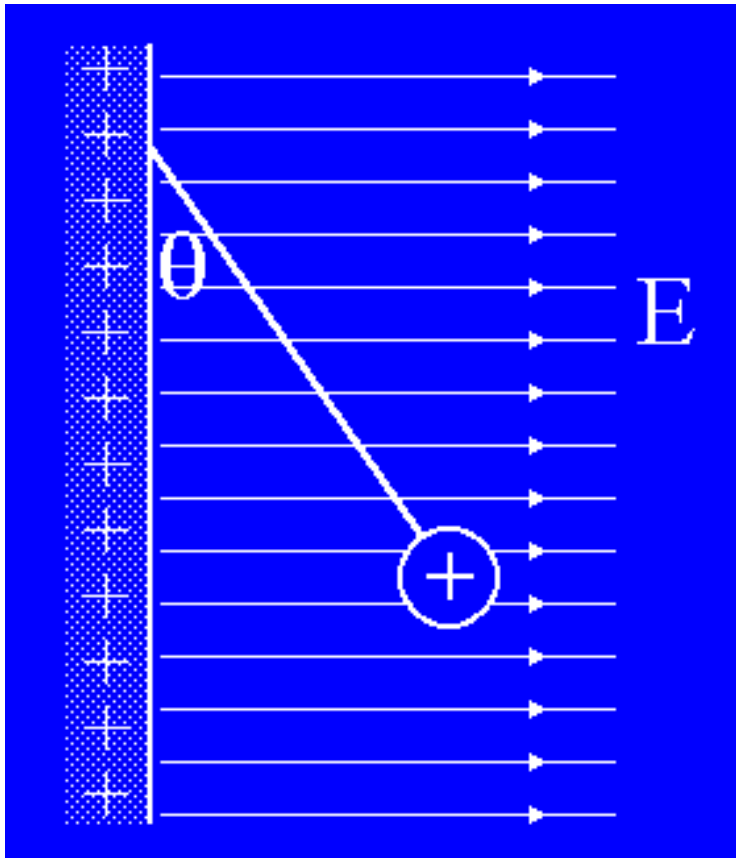


Example



$$T \sin \theta = qE$$

$$T \cos \theta = mg$$

$$\frac{T \sin \theta}{T \cos \theta} = \frac{qE}{mg}$$

$$\tan \theta = \frac{qE}{mg}$$

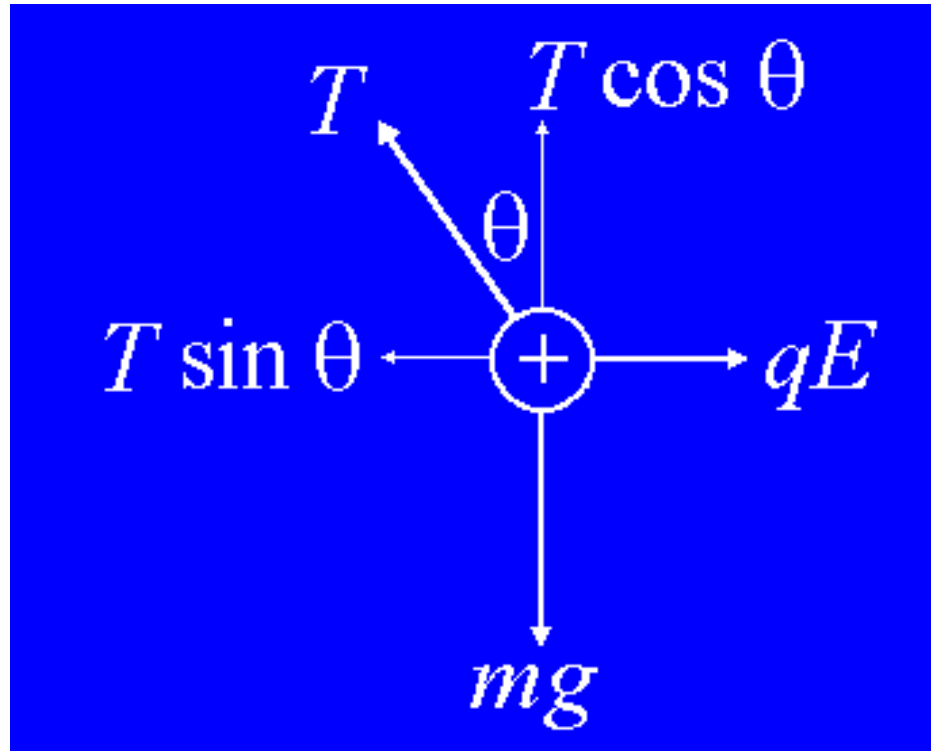


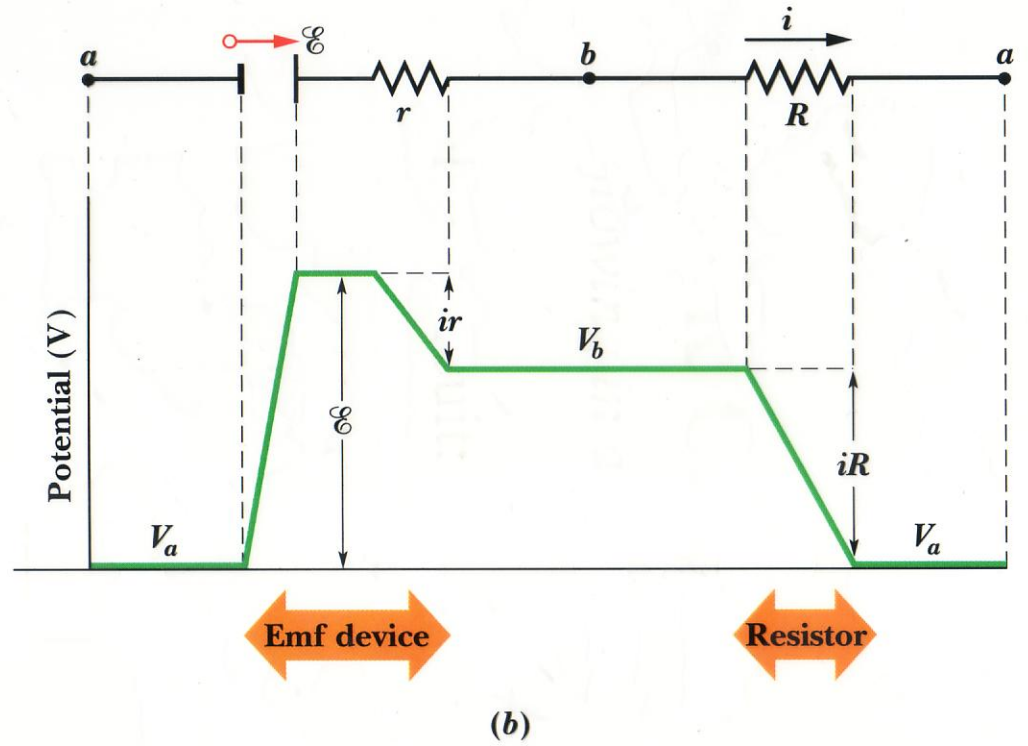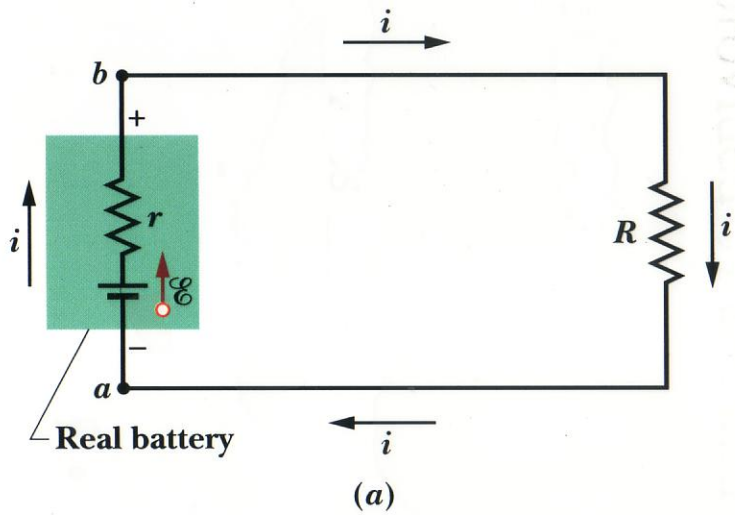

Electric Circuits

“Current flowing in a loop or loops”

Simple, single loop circuit:

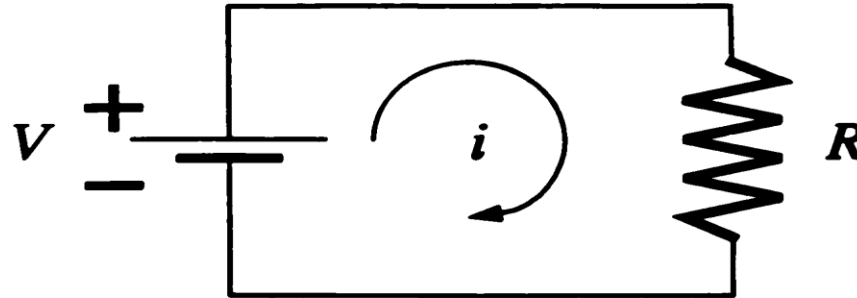


The voltage V is provided by an “emf device”.

By Ohm’s law, we have $V=iR$.

Some lingo:

“The voltage drop across the resistor is iR ”


For multiloop circuits, remember:

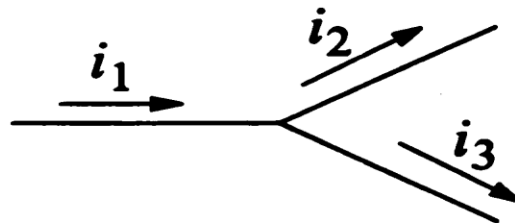

$$i_1 = i_2 + i_3$$

Resistors in Series

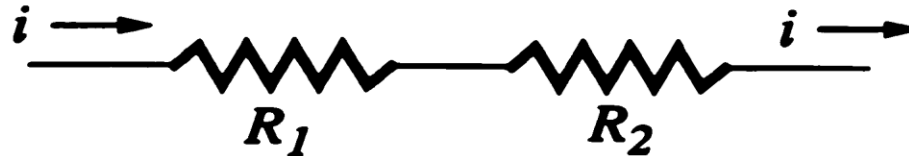If you have two resistors connected in series ...



... then the total voltage drop across them is ...

$$V = iR_1 + iR_2 = i(R_1 + R_2) = iR_{eq}$$


... where

$$R_{eq} = R_1 + R_2$$

“To find the equivalent resistance of two resistors connected in series, just add the two resistances.”

Resistors in Parallel

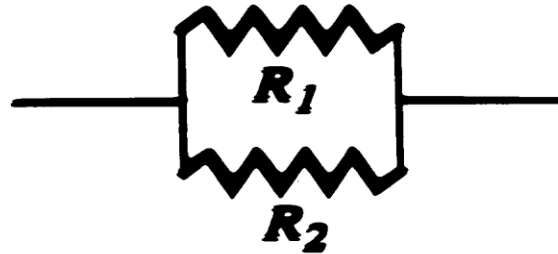If you have two resistors connected in parallel ...



... then the voltage drop across each of them is ...

$$V = i_1 R_1 = i_2 R_2$$

... and we can write ...

$$i = i_1 + i_2 = V \left(\frac{1}{R_1} + \frac{1}{R_2} \right) = \frac{V}{R_{eq}}$$

where the equivalent resistance is given by

$$\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2}$$

“To find the equivalent (reciprocal) resistance of two resistors connected in parallel, add the reciprocals of the two resistances.”

Light Bulbs

Light bulbs are just glowing resistors.

They glow because they get very hot.


The heat energy is radiated away as light.

The brightness of the light is pretty much the same as the power that is radiated away, so

$$\text{Brightness} \approx P = \frac{V^2}{R} = i^2 R$$

Concept Test

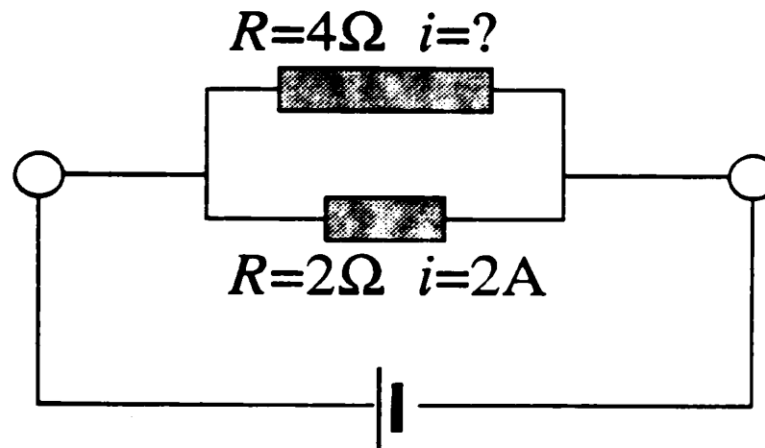
A constant potential V is applied across two resistors connected in parallel as shown.



The current through the 2Ω resistor is $2A$. What is the current through the 4Ω resistor?

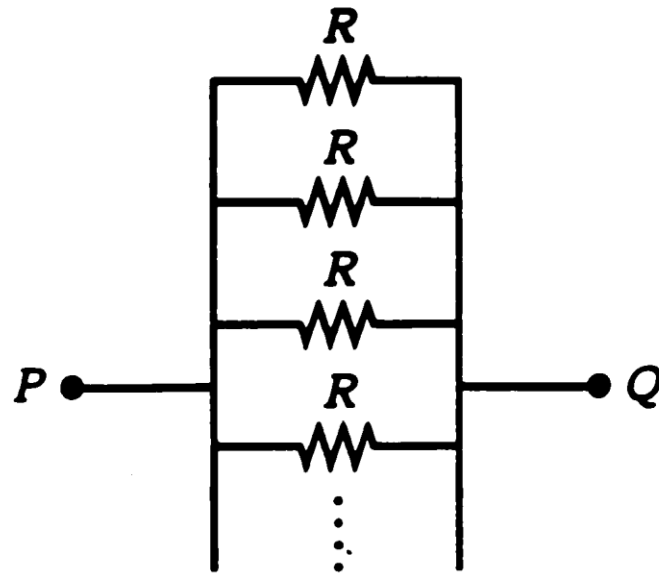1. $0A$
2. $1A$
3. $2A$
4. $4A$
5. Need to know the voltage


As more identical resistors R are added to the parallel circuit shown here, the total resistance between points P and Q




1. increases.
2. remains the same.
3. decreases.

If the four light bulbs in the figure are identical, which circuit puts out more light?

circuit I

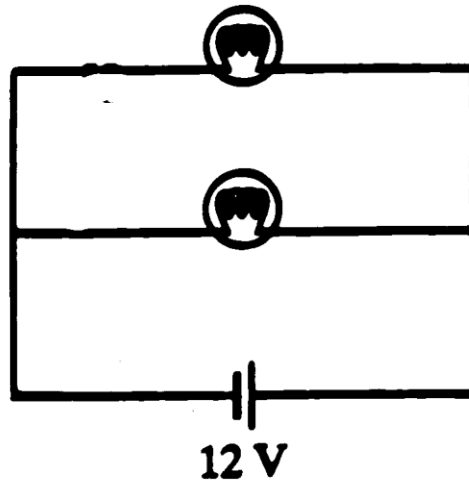


circuit II

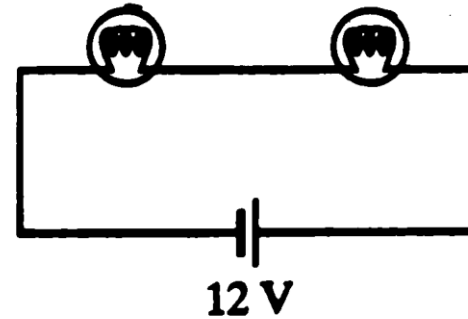

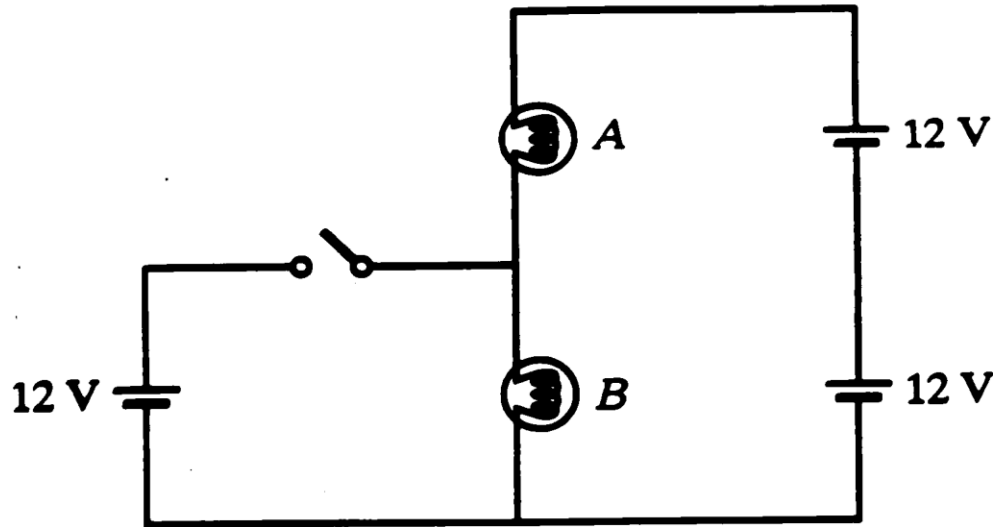
1. I.
2. The two emit the same amount of light.
3. II.

The light bulbs in the circuit are identical.
When the switch is closed,



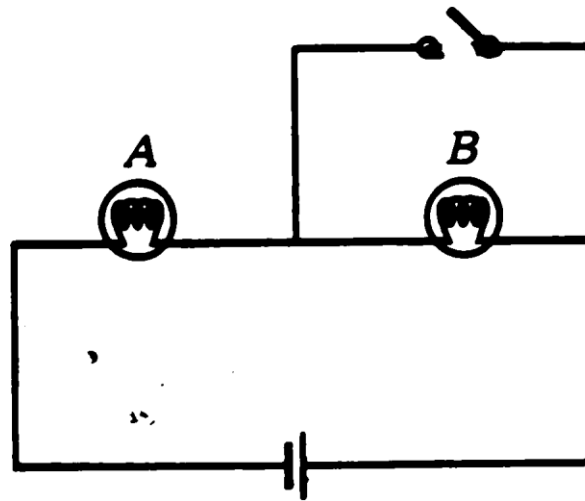1. both go out.
2. the intensity of light bulb *A* increases.
3. the intensity of light bulb *A* decreases.
4. the intensity of light bulb *B* increases.
5. the intensity of light bulb *B* decreases.
6. some combination of 1–5 occurs.
7. nothing changes.

The circuit below consists of two identical light bulbs burning with equal brightness and a single 12 V battery. When the switch is closed, the brightness of bulb A



1. increases.
2. remains unchanged.
3. decreases.

Concept Test

A battery is connected to a 5Ω resistor which is immersed in water. The current through the resistor heats the water by 10°F in 10 minutes. If the 5Ω resistor is replaced by a 10Ω resistor, the water temperature increases by 10°F in

1. 2.5 minutes
2. 5 minutes
3. 10 minutes
4. 20 minutes
5. 40 minutes

Consider two identical resistors wired in series (one behind the other). If there is an electric current through the combination, the current in the second resistor is

- 1. equal to**
- 2. half**
- 3. smaller than, but not necessarily half**

the current through the first resistor.